

Physics Challenge for Teachers and Students


Boris Korsunsky, Column Editor
Weston High School, Weston, MA 02493
korsunbo@post.harvard.edu

Solution to April 2016 Challenge

► Back to square one

A circuit below consists of four resistors connected by ideal wires. The circuit draws power P if an ideal battery is connected to either points A and D or points B and C. If the same battery is connected to either points A and B or points C and D, the circuit draws power $2P$.

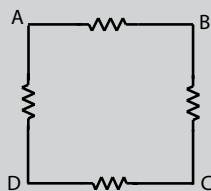What power would be drawn if the same battery is connected to points A and C?



Solution:

Let's use the following designations:

$$R_{AB} = R_1$$

$$R_{BC} = R_2$$

$$R_{CD} = R_3$$

$$R_{DA} = R_4$$

If an ideal battery (ε) is connected to the points A and D, the equivalent resistance is

$$R_{eq1} = \frac{1}{\frac{1}{R_4} + \frac{1}{R_1 + R_2 + R_3}} \quad (1)$$

If an ideal battery (ε) is connected to the points B and C, the equivalent resistance is

$$R_{eq2} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_1 + R_4 + R_3}} \quad (2)$$

In both cases, the circuit draws power P :

$$P = \frac{\varepsilon^2}{R_{eq}}$$

So,

$$\frac{\varepsilon^2}{P} = R_{eq1}$$

$$\frac{\varepsilon^2}{P} = R_{eq2}$$

It means that:

$$R_{eq1} = R_{eq2}$$

Finally, by using Eqs. (1) and (2), we obtain:

$$R_2 = R_4 \quad (3)$$

In the same way, if an ideal battery (ε) is connected to the points A and B, the equivalent resistance is

$$R_{eq3} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2 + R_3 + R_4}} \quad (4)$$

If an ideal battery (ε) is connected to the points C and D, the equivalent resistance is

$$R_{eq4} = \frac{1}{\frac{1}{R_3} + \frac{1}{R_1 + R_2 + R_4}} \quad (5)$$

In that case, the circuit draws power $2P$

$$2P = \frac{\varepsilon^2}{R_{eq}}$$

So,

$$\frac{\varepsilon^2}{2P} = R_{eq3} \quad \text{and} \quad \frac{\varepsilon^2}{2P} = R_{eq4}$$

It means that:

$$R_{eq3} = R_{eq4}$$

Finally, by using Eqs. (4) and (5), we obtain:

$$R_1 = R_3 \quad (6)$$

By using the result of Eqs. (3) and (6) in Eqs. (1) and (2), we obtain:

$$R_{eq1} = R_{eq2} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_2 + 2R_1}} = \frac{\varepsilon^2}{P} \quad (7)$$

By using the result of Eqs. (3) and (6) in Eqs. (4) and (5), we obtain:

$$R_{eq3} = R_{eq4} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_1 + 2R_2}} = \frac{\varepsilon^2}{2P} \quad (8)$$

Taking Eqs. (7) and (8), we obtain:

$$R_2 = R_1(1 + \sqrt{3}) \quad (9)$$

By substitution of the result of Eq. (9) in Eq. (8), we obtain:

$$\frac{\varepsilon^2}{P} = \frac{3 + 2\sqrt{3}}{2 + \sqrt{3}} R_1$$

$$\frac{\varepsilon^2}{R_1} = \frac{3 + 2\sqrt{3}}{2 + \sqrt{3}} P. \quad (10)$$

If the same battery is connected to points A and C, the equivalent resistance would be:

$$R_p = \frac{R_1(2 + \sqrt{3})}{2}. \quad (11)$$

In that case, the circuit draws power:

$$P_T = \frac{\varepsilon^2}{R_p}. \quad (12)$$

By using Eqs. (10), (11), and (12), we obtain the final solution:

$$P_T = 2(2\sqrt{3} - 3)P \approx 0.928 P.$$

(Submitted by José Antonio Santiago Espinal, student, Escuela Politécnica Superior University of Seville, Seville, Spain)

We also recognize the following successful contributors:

Wayne R. Anderson (Sacramento City College, Sacramento, California, emeritus)

Philip Blanco (Grossmont College, El Cajon, CA)

Phil Cahill (The SI Organization, Inc., Rosemont, PA)

David A. Cornell (emeritus, Principia College, Elsau, IL)

Don Easton (Lacombe, Alberta, Canada)

Supriyo Ghosh (Kolkata, India)

Fredrick P. Gram (Cuyahoga Community College, Cleveland, OH)

Gerald E. Hite (TAMUG, Galveston, TX)

Charles Holbrow (emeritus, Colgate University, Hamilton, NY)

Art Hovey (Galvanized Jazz Band, Milford, CT)

José Ignacio Íñiguez de la Torre (Universidad de Salamanca, Salamanca, Spain)

John Mallinckrodt (Cal Poly Pomona, Pomona, CA)

Stephen McAndrew (Sydney, Australia)

Daniel Mixson (Naval Academy Preparatory School, Newport, RI)

Hunter Morris, student (John Tyler Community College, Midlothian, VA)

Carl E. Mungan (U. S. Naval Academy, Annapolis, MD)

Thomas Olsen (Dar Al Uloom University, College of Medicine; Riyadh, Saudi Arabia)

Jacob Owens (John Tyler Community College, Midlothian, VA)

Michael Pocius, student (John Tyler Community College, Midlothian, VA)

Pascal Renault (John Tyler Community College, Midlothian, VA)

Daniel Schumayer (University of Otago, Dunedin, New Zealand)

Robert Siddon (U. S. Naval Academy, Annapolis, MD)

Jason L. Smith (Richland Community College, Decatur, IL)

Clint Sprott (University of Wisconsin – Madison, WI)

Michael Wood (National Institute of Standards and Technology)

Wu Yonghao (Tian Yi High School, Wuxi, Jiangsu province, China)

Guidelines for contributors:

- We ask that all solutions, preferably in Word format, be submitted to the dedicated email address challenges@aapt.org. Each message will receive an automatic acknowledgment.
- The subject line of each message should be the same as the name of the solution file (see the instructions below).
- The deadline for submitting the solutions is the last day of the corresponding month.
- We can no longer guarantee that we'll publish every successful solver's name; each month, a representative selection of names will be published, both in print and on the web.
- If your name is—for instance—Donald Duck, please name the file "**Duck16May**" (do not include your first initial) when submitting the May 2016 solution.
- If you have a message for the Column Editor, you may contact him at korsunbo@post.harvard.edu; however, please do not send your solutions to this address.

As always, we look forward to your contributions and hope that they will include not only solutions but also your own Challenges that you wish to submit for the column.

Many thanks to all contributors and we hope to hear from many more of you in the future!

–Boris Korsunsky